


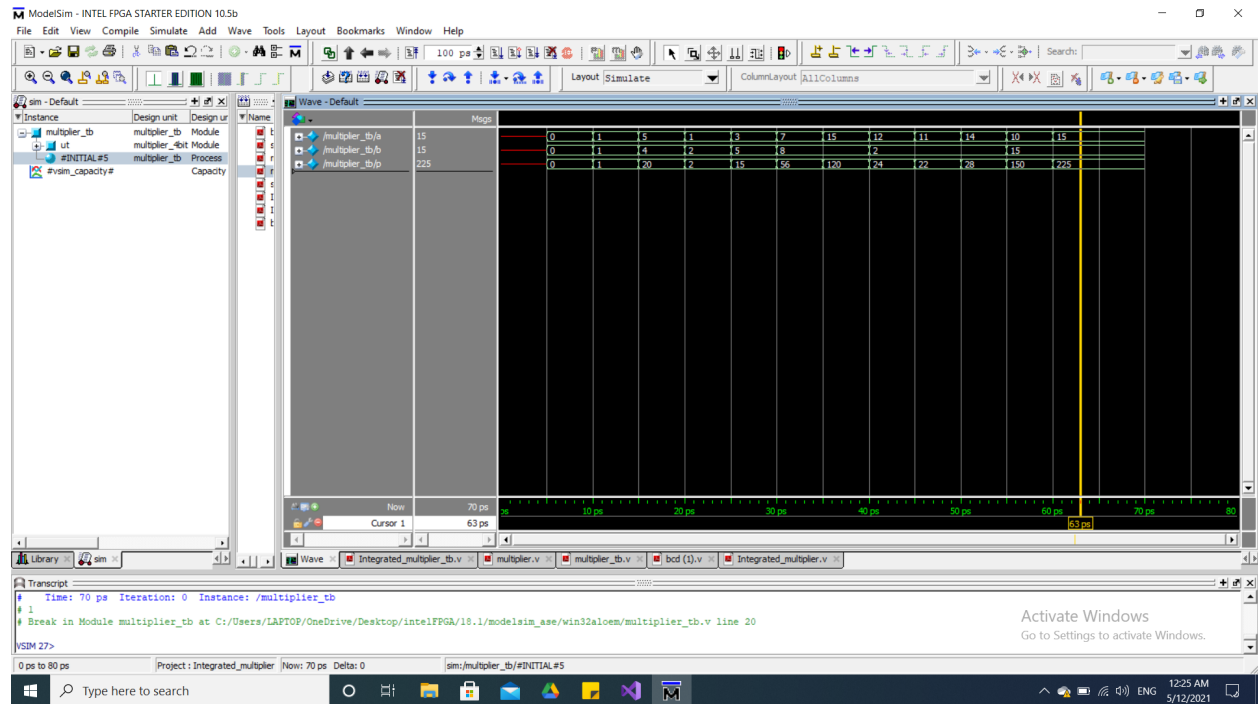




# Multiplier

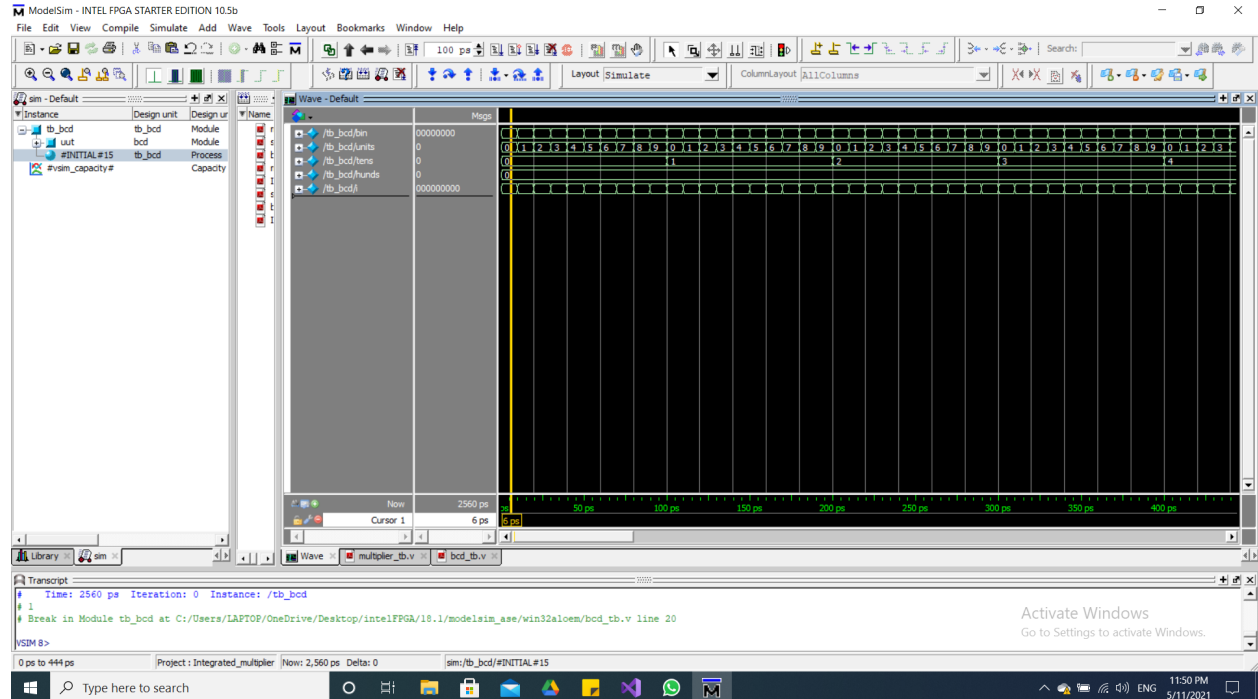


# BCD encoder

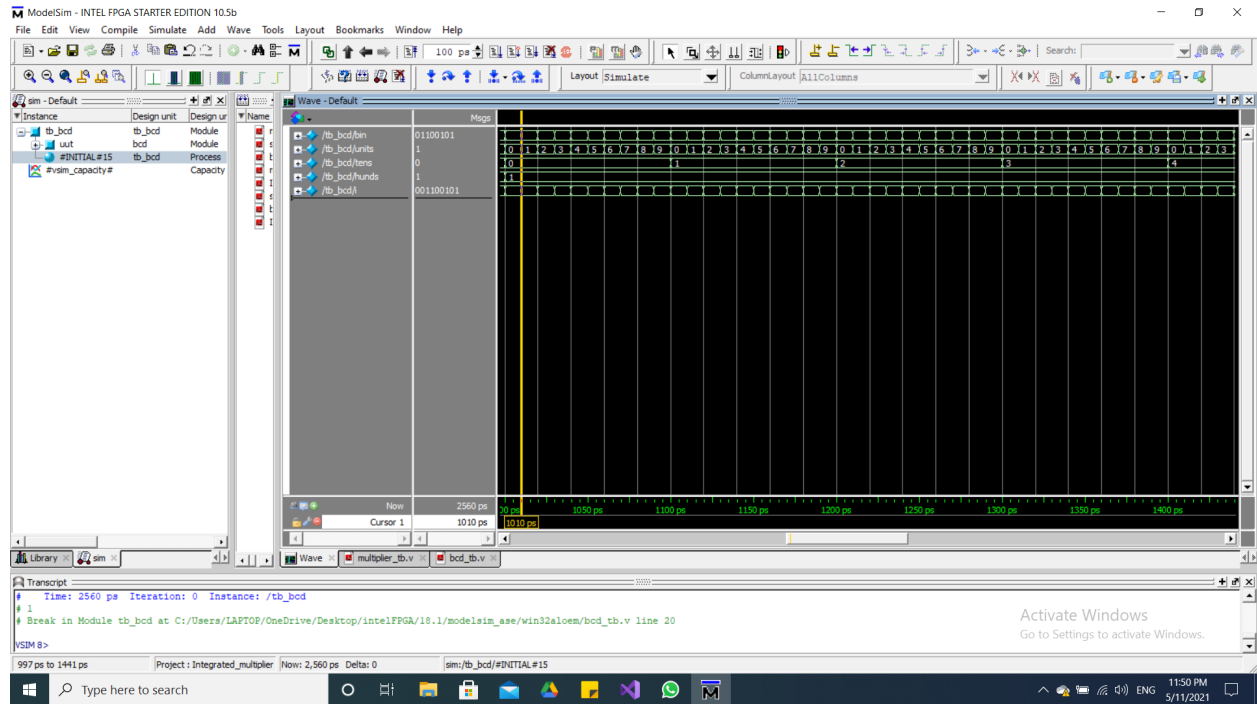


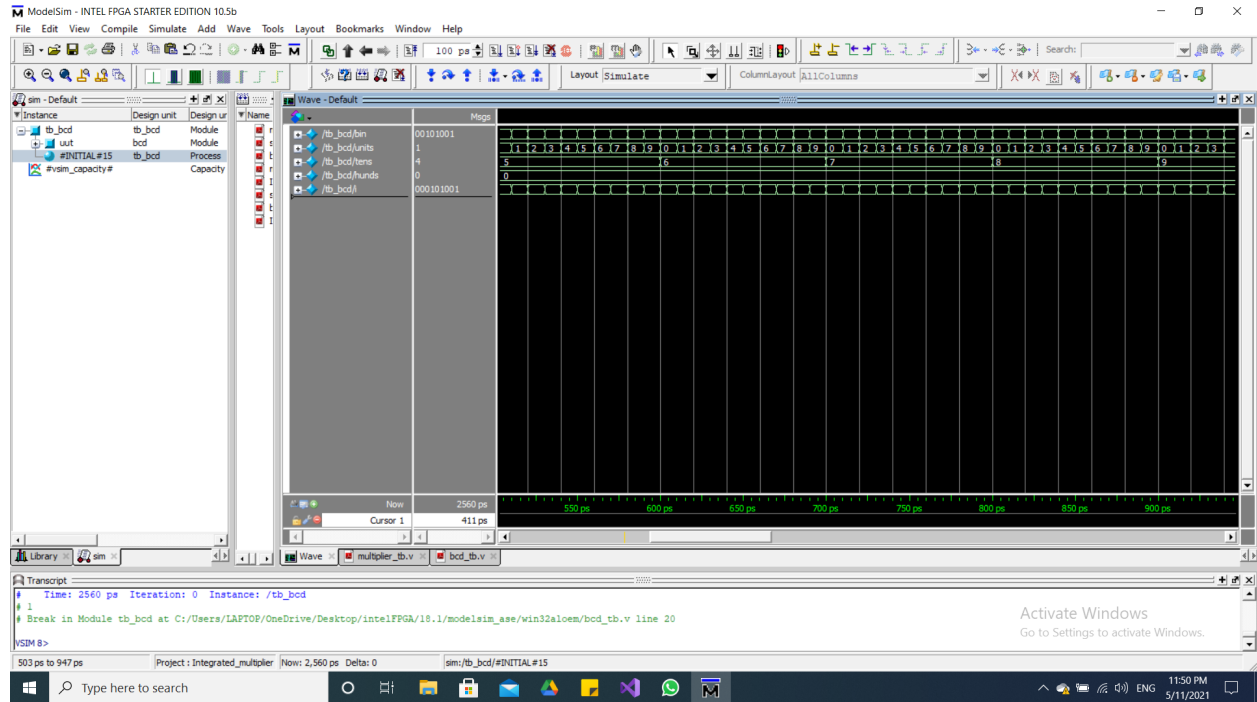


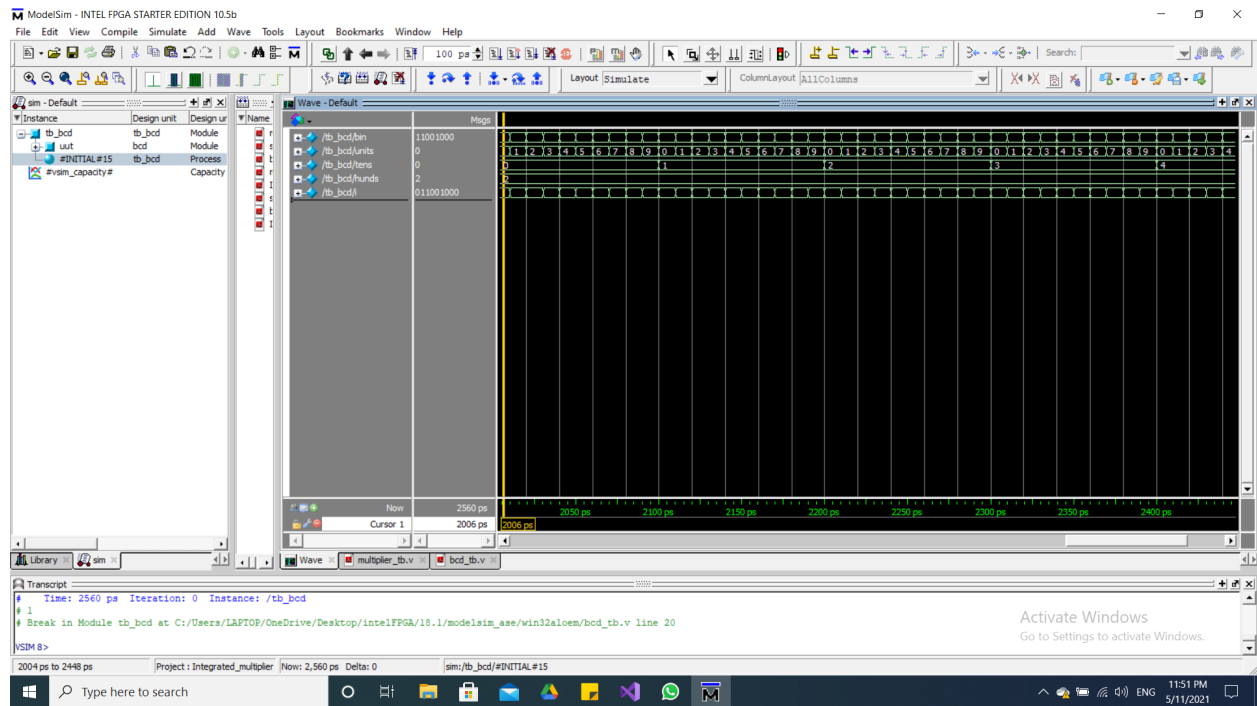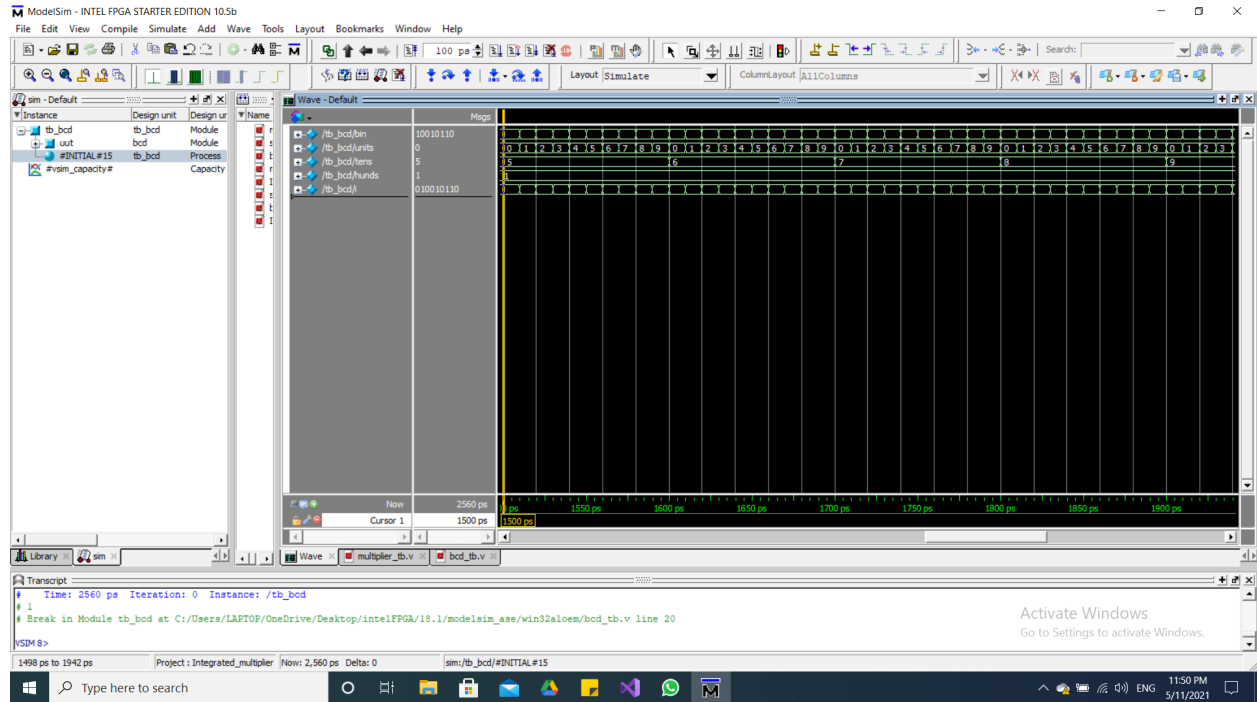

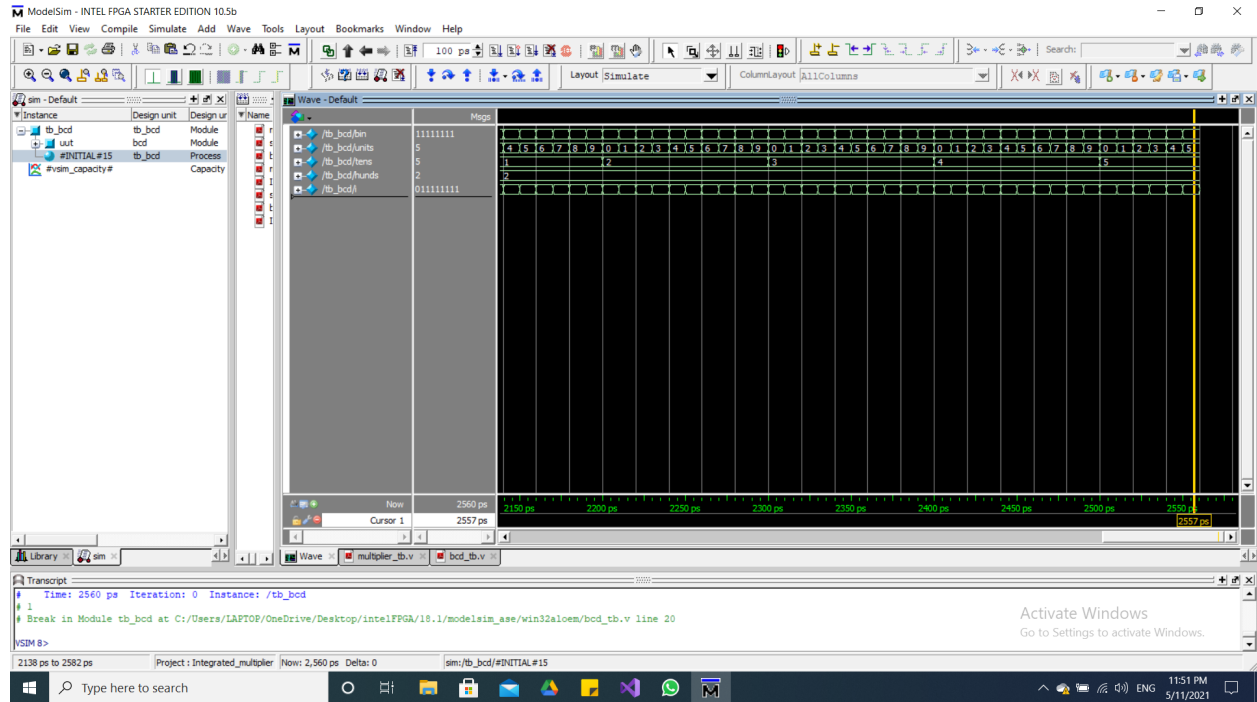

## Seven-Segment Decoder

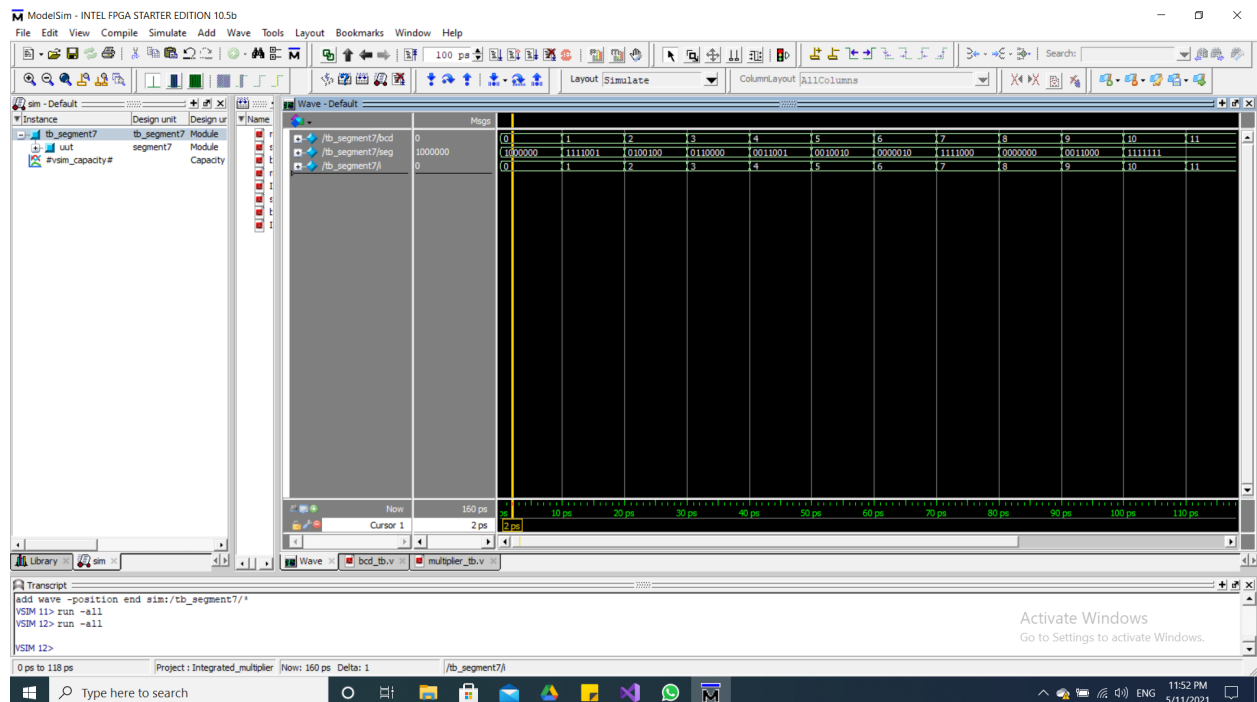

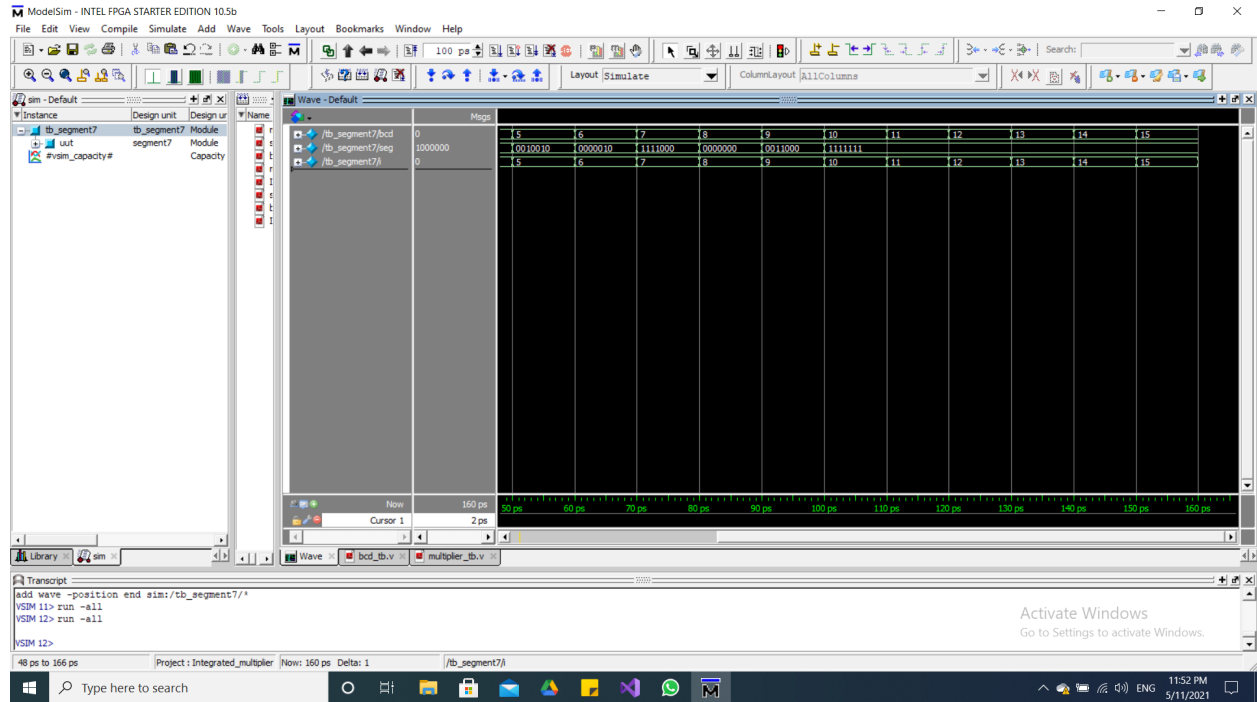

## Integrated Multiplier

